





دانشگاه پیام نور مرکز ملایر

فصل پنجم

مجموعه مثال های کاربردی از

VHDL

ترم بهار ۹۷-۹۶

دانشگاه پیام نور مرکز ملایر

دانشکده فنی و مهندسی

مهندسی کامپیوتر گرایش نرم افزار

عنوان درس: طراحی کامپیوتری سیستمهای دیجیتال

استاد راهنما: سرکار خانم مهندس بابایی

دروازه های منطقی پایه:

- هر توصیف طرح به زبان VHDL شامل حداقل یک جفت ENTITY / ARCHITECTURE یا یک ENTITY یا ARCHITECTURE تعدادی ARCHITECTURE می باشد. بخش ENTITY برای تعریف درگاه های ورودی خروجی مدار استفاده میشود در حالی که کد توصیف مدار در ARCHITECTURE قرار گرفته است. توصیف مدار با استفاده از دستورات مختلف زبان VHDL و به روشهای مختلف صورت میگیرد. در این بخش انواع دروازه های منطقی را ملاحظه خواهید کرد.

EXAMPLE(5-1): DRIVER

توصیف یک درایور (بافر)

```
-----  
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
-----  
ENTITY DRIVER IS  
PORT( X: IN STD_LOGIC;  
      F: OUT STD_LOGIC );  
END DRIVER;  
-----  
ARCHITECTURE BEHV2 OF DRIVER IS  
BEGIN  
    F <= X;  
END BEHV2;  
-----
```

EXAMPLE(5-1): DRIVER

```
ENTITY DRIVER IS
PORT( X: IN STD_LOGIC;
      F: OUT STD_LOGIC );
END DRIVER;
```

```
ARCHITECTURE BEHV1 OF DRIVER IS
BEGIN
    PROCESS (X)
    BEGIN
        -- COMPARE TO TRUTH TABLE
        IF (X='1') THEN
            F <= '1';
        ELSE
            F <= '0';
        END IF;
    END PROCESS;
END BEHV1;
```

F <= X;

EXAMPLE(5-3): AND GATE

توصیف دروازه AND دو

ورودی

```
-----  
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
-----  
ENTITY AND_ENT IS  
PORT( X: IN STD_LOGIC;  
      Y: IN STD_LOGIC;  
      F: OUT STD_LOGIC );  
END AND_ENT;  
-----  
ARCHITECTURE BEHAV2 OF AND_ENT IS  
BEGIN  
    F <= X AND Y;  
END BEHAV2;  
-----
```

EXAMPLE(5-3): AND GATE

```
ENTITY AND_ENT IS
PORT ( X: IN STD_LOGIC;
       Y: IN STD_LOGIC;
       F: OUT STD_LOGIC );
END AND_ENT;
```

```
ARCHITECTURE BEHAV1 OF AND_ENT IS
BEGIN
    PROCESS (X, Y)
    BEGIN
        -- COMPARE TO TRUTH TABLE
        IF ((X='1') AND (Y='1')) THEN
            F <= '1';
        ELSE
            F <= '0';
        END IF;
    END PROCESS;
END BEHAV1;
```

$F \leq x \text{ and } y;$

NOR دو ورودی یک توصیف یک EXAMPLE(5-6): NOR GATE

```
-----  
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
-----  
ENTITY NOR_ENT IS  
PORT( X: IN STD_LOGIC;  
      Y: IN STD_LOGIC;  
      F: OUT STD_LOGIC);  
END NOR_ENT;  
-----  
ARCHITECTURE BEHV2 OF NOR_ENT IS  
BEGIN  
    F <= X NOR Y;  
END BEHV2;  
-----
```


EXAMPLE(5-6): NOR GATE

```
ENTITY NOR_ENT IS
PORT (   X: IN STD_LOGIC;
        Y: IN STD_LOGIC;
        F: OUT STD_LOGIC);
END NOR_ENT;
```

```
ARCHITECTURE BEHV1 OF NOR_ENT IS
BEGIN
    PROCESS (X, Y)
    BEGIN
        -- COMPARE TO TRUTH TABLE
        IF (X='0' AND Y='0') THEN
            F <= '1';
        ELSE
            F <= '0';
        END IF;
    END PROCESS;
END BEHV1;
```

$F \leq x \text{ nor } y;$

دو XOR یک توصیف EXAMPLE(5-7): XOR GATE

ورودی

```
-----  
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
-----  
ENTITY XOR_ENT IS  
PORT( X: IN STD_LOGIC;  
      Y: IN STD_LOGIC;  
      F: OUT STD_LOGIC);  
END XOR_ENT;  
-----  
ARCHITECTURE BEHV2 OF XOR_ENT IS  
BEGIN  
    F <= X XOR Y;  
END BEHV2;  
-----
```

EXAMPLE(5-8): XNOR

توصیف یک XNOR دو

ورودی

```
-----  
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
-----  
ENTITY XNOR_ENT IS  
PORT( X: IN STD_LOGIC;  
      Y: IN STD_LOGIC;  
      F: OUT STD_LOGIC);  
END XNOR_ENT;  
-----  
ARCHITECTURE BEHV2 OF XNOR_ENT IS  
BEGIN  
    F <= X XNOR Y;  
END BEHV2;  
-----
```

EXAMPLE(5-8): XNOR

```
ENTITY XNOR_ENT IS
PORT ( X: IN STD_LOGIC;
      Y: IN STD_LOGIC;
      F: OUT STD_LOGIC);
END XNOR_ENT;
```

```
ARCHITECTURE BEHV1 OF XNOR_ENT IS
BEGIN
    PROCESS (X, Y)
    BEGIN
        -- COMPARE TO TRUTH TABLE
        IF (X/=Y) THEN
            F <= '0';
        ELSE
            F <= '1';
        END IF;
    END PROCESS;
END BEHV1;
```

F <= x xnor y;

8_BIT TRI_STATE DRIVER بافر سه حالتہ ۸ بیتی

```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY TRISTATE_DR IS  
PORT( D_IN: IN STD_LOGIC_VECTOR(7 DOWNTO 0);  
      EN: IN STD_LOGIC;  
      D_OUT: OUT STD_LOGIC_VECTOR(7 DOWNTO 0) );  
END TRISTATE_DR;
```

```
ARCHITECTURE BEHAVIOR OF TRISTATE_DR IS  
BEGIN  
    D_OUT <= D_IN WHEN EN='1' ELSE "ZZZZZZZZ";  
END BEHAVIOR;
```

مثال ۵-۱۱) مالتی پلکسر ۴ به ۱ سے بیٹی

```
ENTITY MUX IS
PORT( I3:      IN STD_LOGIC_VECTOR(2 DOWNTO 0);
      I2:      IN STD_LOGIC_VECTOR(2 DOWNTO 0);
      I1:      IN STD_LOGIC_VECTOR(2 DOWNTO 0);
      I0:      IN STD_LOGIC_VECTOR(2 DOWNTO 0);
      S:       IN STD_LOGIC_VECTOR(1 DOWNTO 0);
      O:       OUT STD_LOGIC_VECTOR(2 DOWNTO 0));
END MUX;
```

```
-----
ARCHITECTURE BEHV1 OF MUX IS
BEGIN
    PROCESS (I3, I2, I1, I0, S)
    BEGIN
        -- USE CASE STATEMENT
        CASE S IS
            WHEN "00" =>          O <= I0;
            WHEN "01" =>          O <= I1;
            WHEN "10" =>          O <= I2;
            WHEN "11" =>          O <= I3;
            WHEN OTHERS =>        O <= "ZZZ";
        END CASE;
    END PROCESS;
END BEHV1;
```

مثال ۵-۱۱) مالتی پلکسر ۴ به ۱ سه بیتی

```
ENTITY MUX IS
PORT ( I3:      IN STD_LOGIC_VECTOR(2 DOWNTO 0);
      I2:      IN STD_LOGIC_VECTOR(2 DOWNTO 0);
      I1:      IN STD_LOGIC_VECTOR(2 DOWNTO 0);
      I0:      IN STD_LOGIC_VECTOR(2 DOWNTO 0);
      S:       IN STD_LOGIC_VECTOR(1 DOWNTO 0);
      O:       OUT STD_LOGIC_VECTOR(2 DOWNTO 0));
END MUX;
```

```
ARCHITECTURE BEHV2 OF MUX IS
BEGIN
```

```
    -- USE WHEN.. ELSE STATEMENT
```

```
    O <=      I0 WHEN S="00" ELSE
              I1 WHEN S="01" ELSE
              I2 WHEN S="10" ELSE
              I3 WHEN S="11" ELSE
              "ZZZ";
```

```
END BEHV2;
```

مثال ۵-۱۴) مقایسه کننده N بیتی

```
-- EXAMPLE (5-14) : N-BIT COMPARATOR  
-- TWO N-BIT INPUTS & THREE 1-BIT OUTPUTS
```

```
LIBRARY IEEE;
```

```
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY COMPARATOR IS
```

```
GENERIC (N: NATURAL :=2);
```

```
PORT ( A:IN STD_LOGIC_VECTOR(N-1 DOWNT0 0);
```

```
      B:IN STD_LOGIC_VECTOR(N-1 DOWNT0 0);
```

```
      LESS:OUT STD_LOGIC;
```

```
      EQUAL:OUT STD_LOGIC;
```

```
      GREATER:OUT STD_LOGIC);
```

```
END COMPARATOR;
```


مثال ۵-۱۴) مقایسه کننده N بیتی

```
ARCHITECTURE BEHV OF COMPARATOR IS
BEGIN
    PROCESS (A, B)
    BEGIN
        IF (A<B) THEN
            LESS <= '1';
            EQUAL <= '0';
            GREATER <= '0';
        ELSIF (A=B) THEN
            LESS <= '0';
            EQUAL <= '1';
            GREATER <= '0';
        ELSE
            LESS <= '0';
            EQUAL <= '0';
            GREATER <= '1';
        END IF;
    END PROCESS;
END BEHV;
```

طراحی مدارات ترتیبی و ماشین حالت

- مدارات ترتیبی شامل:
 - سیگنالهای ورودی
 - سیگنالهای خروجی
 - سیگنال کلاک
- احیانا یکسری سیگنالهای کنترلی دیگر (مانند RESET)
- سیگنالهای کنترلی می توانند فعال صفر یا یک باشند
- انتقال از یک وضعیت به وضعیت دیگر لبه سیگنال کلاک
- (CLOCK 'EVENT AND CLOCK='1')
- (CLOCK 'EVENT AND CLOCK='0')

مثال ۵-۱۷) نگهدار D

```
ENTITY D LATCH IS
PORT( DATA_IN:      IN STD_LOGIC;
      ENABLE:        IN STD_LOGIC;
      DATA_OUT:     OUT STD_LOGIC );
END D_LATCH;
```

```
ARCHITECTURE BEHV OF D_LATCH IS
BEGIN
  --COMPARE THIS TO D FLIPFLOP
  PROCESS (DATA_IN, ENABLE)
  BEGIN
    IF (ENABLE='1') THEN
      --NO CLOCK SIGNAL HERE
      DATA_OUT <= DATA_IN;
    END IF;
  END PROCESS;
END BEHV;
```

مثال ۵-۱۸) فیلیپ فلاپ D

```
ENTITY DFF IS
PORT ( DATA_IN:      IN STD_LOGIC;
      CLOCK:          IN STD_LOGIC;
      DATA_OUT:     OUT STD_LOGIC);
END DFF;
```

```
ARCHITECTURE BEHV OF DFF IS
BEGIN
  PROCESS (DATA_IN, CLOCK)
  BEGIN
    -- CLOCK RISING EDGE
    IF (CLOCK='1' AND CLOCK'EVENT) THEN
      DATA_OUT <= DATA_IN;
    END IF;
  END PROCESS;
END BEHV;
```

مثال ۵-۲۱

ثبات انتقالی

```
ENTITY SHIFT_REG IS
PORT ( I:      IN STD_LOGIC;
       CLOCK: IN STD_LOGIC;
       SHIFT:  IN STD_LOGIC;
       Q:      OUT STD_LOGIC );
END SHIFT_REG;
```

```
ARCHITECTURE BEHV OF SHIFT_REG IS
-- INITIALIZE THE DECLARED SIGNAL
SIGNAL S: STD_LOGIC_VECTOR(2 DOWNTO 0) := "111";
BEGIN
PROCESS (I, CLOCK, SHIFT, S)
BEGIN
-- EVERYTHING HAPPENS UPON THE CLOCK CHANGING
IF CLOCK'EVENT AND CLOCK='1' THEN
    IF SHIFT = '1' THEN
        S <= I & S(2 DOWNTO 1);
    END IF;
END IF;
END PROCESS;
-- CONCURRENT ASSIGNMENT
Q <= S(0);
END BEHV;
```

```
-----  
ENTITY COUNTER IS  
  GENERIC(N: NATURAL :=2);  
  PORT(   CLOCK: IN STD_LOGIC;  
         CLEAR: IN STD_LOGIC;  
         COUNT: IN STD_LOGIC;  
         Q:    OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0));  
END COUNTER;
```

مثال ۵-۲۲


شمارنده N

بیتی

```
-----  
ARCHITECTURE BEHV OF COUNTER IS  
  SIGNAL PRE_Q: STD_LOGIC_VECTOR(N-1 DOWNT0 0);  
BEGIN  
  -- BEHAVIOR DESCRIBE THE COUNTER  
  PROCESS(CLOCK, COUNT, CLEAR)  
  BEGIN  
    IF CLEAR = '1' THEN  
      PRE_Q <= PRE_Q - PRE_Q;  
    ELSIF (CLOCK='1' AND CLOCK'EVENT) THEN  
      IF COUNT = '1' THEN  
        PRE_Q <= PRE_Q + 1;  
      END IF;  
    END IF;  
  END PROCESS;  
  -- CONCURRENT ASSIGNMENT STATEMENT  
  Q <= PRE_Q;  
END BEHV;
```

مثال 5-23) ماشین حالت مور

 مقدار خروجی آن فقط وابسته به حالت فعلی است
هیچ ورودی دخالت مستقیم در عبارت بولی خروجی ها ندارد



حالت فعلی	حالت بعدی		خروجی
	X=0	X=1	
S0	S0	S2	0
S1	S0	S2	1
S2	S2	S3	1
S3	S3	S1	0

```

ENTITY MOORE IS -- MOORE MACHINE
  PORT(X, CLOCK: IN BIT;
        Z: OUT BIT);
END MOORE;

```

مثال (23-5) ماشين حالت مور

```

ARCHITECTURE BEHAVIOR OF MOORE IS
  TYPE STATE_TYPE IS (S0, S1, S2, S3);
  SIGNAL CURRENT_STATE, NEXT_STATE: STATE_TYPE;
BEGIN

```

```

-- PROCESS TO HOLD COMBINATIONAL LOGIC

```

```


COMBIN: PROCESS(CURRENT_STATE, X)
BEGIN

```

```

  CASE CURRENT_STATE IS
    WHEN S0 =>
      Z <= '0';
      IF X = '0' THEN
        NEXT_STATE <= S0;
      ELSE
        NEXT_STATE <= S2;
      END IF;
    WHEN S1 =>
      Z <= '1';
      IF X = '0' THEN
        NEXT_STATE <= S0;
      ELSE
        NEXT_STATE <= S2;
      END IF;

```

 



```

WHEN S2 =>
  Z <= '1';
  IF X = '0' THEN
    NEXT_STATE <= S2;
  ELSE
    NEXT_STATE <= S3;
  END IF;
WHEN S3 =>
  Z <= '0';
  IF X = '0' THEN
    NEXT_STATE <= S3;
  ELSE
    NEXT_STATE <= S1;
  END IF;
END CASE;
END PROCESS COMBIN;

```

ماشین حالت مور

 

```

-----
-- PROCESS TO HOLD SYNCHRONOUS ELEMENTS (FLIP-FLOPS)
SYNCH: PROCESS
BEGIN
  WAIT UNTIL CLOCK'EVENT AND CLOCK = '1';
  CURRENT_STATE <= NEXT_STATE;
END PROCESS SYNCH;
END BEHAVIOR;
-----

```

مثال ۵-۲۵) آشکارساز توالی بیت (ماشین مور)

- توصیف رفتاری یک ماشین حالت از نوع مور
- هدف: تشخیص رشته ی بیتی "1110101101" است
- هر آشکارساز توالی N بیتی به روش مور $N+1$ حالت مورد نیاز دارد
- چون ۱۰ بیت داریم ۱۱ حالت در نظر می گیریم

```
-----  
ENTITY SEQDETECTOR IS  
PORT (CLK, RESET :IN STD_LOGIC;  
      INPUT :IN STD_LOGIC;  
      OUTPUT :OUT STD_LOGIC );  
END SEQDETECTOR ;  
-----
```

```
ARCHITECTURE STAT OF SEQDETECTOR IS  
TYPE STATE_TYPE IS (S0, S1, S2, S3, S4, S5, S6, S7, S8, S9, S10);  
SIGNAL STATE, NEXT_STATE : STATE_TYPE;  
BEGIN  
-----
```

```
STATE_REGISTER: PROCESS (CLK, RESET)  
BEGIN  
  IF RESET = '0' THEN  
    STATE <= S0;  
    OUTPUT<='0';  
  ELSIF CLK'EVENT AND CLK = '1' THEN  
    STATE <= NEXT_STATE;  
  END IF;  
END PROCESS STATE_REGISTER;  
-----
```

مثال 5-25) آشکار ساز توالی بیت

مثال 5-25

آشکار ساز توالی بیت

```
STATE LOGIC : PROCESS ( STATE )
BEGIN
CASE STATE IS
WHEN S0 =>
    OUTPUT<='0';
    IF (INPUT='1') THEN
    NEXT STATE <=S1;
    ELSIF (INPUT='0') THEN
    NEXT STATE <=S0;
    END IF;
WHEN S1 =>
    OUTPUT<='0';
    IF (INPUT='1') THEN
    NEXT STATE <=S2;
    ELSIF (INPUT='0') THEN
    NEXT STATE <=S0;
    END IF;
WHEN S2 =>
    OUTPUT<='0';
    IF (INPUT='1') THEN
    NEXT STATE <=S3;
    ELSIF (INPUT='0') THEN
    NEXT STATE <=S0;
    END IF;
```

--DETECT "11"

--DETECT "111"

مثال 5-25) آشکار ساز توالی بیت

```
WHEN S3 =>                                --DETECT "1110"
OUTPUT<='0';
    IF (INPUT='0') THEN
    NEXT STATE <=S4;
    ELSIF (INPUT='1') THEN
    NEXT STATE <=S2;
    END IF;

WHEN S4 =>                                --DETECT "11101"
OUTPUT<='0';
    IF (INPUT='1') THEN
    NEXT STATE <=S5;
    ELSIF (INPUT='0') THEN
    NEXT STATE <=S0;
    END IF;

WHEN S5 =>                                --DETECT "111010"
OUTPUT<='0';
    IF (INPUT='0') THEN
    NEXT STATE <=S6;
    ELSIF (INPUT='1') THEN
    NEXT STATE <=S2;
    END IF;
```

```

WHEN S6 =>                                --DETECT "1110101"
    OUTPUT<='0';
    IF (INPUT='1') THEN
    NEXT STATE <=S7;
    ELSIF (INPUT='0') THEN
    NEXT STATE <=S0;
    END IF;
WHEN S7 =>                                --DETECT "11101011"
    OUTPUT<='0';
    IF (INPUT='1') THEN
    NEXT STATE <=S8;
    ELSIF (INPUT='0') THEN
    NEXT STATE <=S0;
    END IF;
WHEN S8 =>                                --DETECT "111010110"
    OUTPUT<='0';
    IF (INPUT='0') THEN
    NEXT STATE <=S9;
    ELSIF (INPUT='1') THEN
    NEXT STATE <=S2;
    END IF;

```

مثال 5-25


آشکار ساز توالی بیت

مثال 5-25) آشکار ساز توالی بیت

```
WHEN S9 =>                                --DETECT "1110101101"
    OUTPUT<='0';
    IF (INPUT='1') THEN
        NEXT_STATE <=S10;
    ELSIF (INPUT='1') THEN
        NEXT_STATE <=S0;
    END IF;
WHEN S10 =>                                -- OUTPUT ASSERTED
    OUTPUT<='1';
    NEXT_STATE<=S0;
END CASE;
END PROCESS STATE_LOGIC;
END STAT;
```

مثال 5-26) ماشین میلی

 مقدار خروجی آن وابسته به حالت فعلی و خروجی است



حالت فعلی	حالت بعدی		خروجی	
	X=0	X=1	X=0	X=1
S0	S0	S2	0	1
S1	S0	S2	0	0
S2	S2	S3	1	0
S3	S3	S1	0	1


```
-----  
ENTITY MEALY IS -- MEALY MACHINE  
  PORT(X, CLOCK: IN BIT;  
        Z: OUT BIT);  
END MEALY;
```

مثال (26-5) ماشين ميلي

```
-----  
ARCHITECTURE BEHAVIOR OF MEALY IS  
  TYPE STATE_TYPE IS (S0, S1, S2, S3);  
  SIGNAL CURRENT_STATE, NEXT_STATE: STATE_TYPE;  
BEGIN  
-----  
-- PROCESS TO HOLD COMBINATIONAL LOGIC.  
  COMBIN: PROCESS(CURRENT_STATE, X)  
  BEGIN  
  CASE CURRENT_STATE IS  
  WHEN S0 =>  
    IF X = '0' THEN  
      Z <= '0';  
      NEXT_STATE <= S0;  
    ELSE  
      Z <= '1';  
      NEXT_STATE <= S2;  
    END IF;--  
  WHEN S1 =>  
    IF X = '0' THEN  
      Z <= '0';  
      NEXT_STATE <= S0;  
    ELSE  
      Z <= '0';  
      NEXT_STATE <= S2;  
    END IF;--  
  END  
END COMBIN;
```

مثال 5-26) ماشين ميلي

```
WHEN S2 =>
  IF X = '0' THEN
    Z <= '1';
    NEXT_STATE <= S2;
  ELSE
    Z <= '0';
    NEXT_STATE <= S3;
  END IF;
WHEN S3 =>
  IF X = '0' THEN
    Z <= '0';
    NEXT_STATE <= S3;
  ELSE
    Z <= '1';
    NEXT_STATE <= S1;
  END IF;
END CASE;
END PROCESS COMBIN;
-----
-- PROCESS TO HOLD SYNCHRONOUS ELEMENTS (FLIP-FLOPS)
SYNCH: PROCESS
BEGIN
  WAIT UNTIL CLOCK'EVENT AND CLOCK = '1';
  CURRENT_STATE <= NEXT_STATE;
END PROCESS SYNCH;
END BEHAVIOR;
-----
```

RAM با ورودی و خروجی مجزا

```
-----  
-- Example(5-28): RAM with separated input output  
-- No RD input (output allways enable)  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
-----  
ENTITY ram IS  
  GENERIC ( bits: INTEGER := 8;      -- # of bits per word  
           words: INTEGER := 16); -- # of words in the memory  
  PORT ( wr_ena, clk: IN STD_LOGIC;  
        addr: IN INTEGER RANGE 0 TO words-1;  
        data_in: IN STD_LOGIC_VECTOR (bits-1 DOWNTO 0);  
        data_out: OUT STD_LOGIC_VECTOR (bits-1 DOWNTO 0));  
END ram;  
-----  
ARCHITECTURE ram OF ram IS  
  TYPE vector_array IS ARRAY (0 TO words-1) OF  
    STD_LOGIC_VECTOR(bits-1 DOWNTO 0);  
  signal memory: vector_array;  
BEGIN  
  PROCESS (clk, wr_ena) THEN  
    BEGIN  
      IF (wr_ena='1')  
        IF (clk'EVENT AND clk='1') THEN  
          memory(addr) <= data_in;  
        END IF;  
      END IF;  
    END PROCESS;  
    data_out <= memory(addr);  
END ram;  
-----
```

حافظه فقط خواندنی (ROM)

```
-----  
Example (5-31) : ROM 8x8  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
-----  
ENTITY rom IS  
  GENERIC ( bits: INTEGER := 8;  --# of bits per word  
           words: INTEGER := 8);  --# of words in  
  the memory  
  PORT (Addr  : IN INTEGER RANGE 0 TO words-1;  
        Enable: in std_logic;  
        Read  : in std_logic;  
        Data  : OUT STD_LOGIC_VECTOR(bits-1 DOWNT0 0));  
END rom;  
-----  
ARCHITECTURE rom OF rom IS  
  TYPE vector_array IS ARRAY (0 TO words-1) OF  
    STD_LOGIC_VECTOR (bits-1 DOWNT0 0);  
  ONSTANT memory: vector_array := ("10000000",  
                                     "01000000",  
                                     "00100000",  
                                     "00010000",  
                                     "00001000",  
                                     "00000100",  
                                     "00000010",  
                                     "00000001");  
BEGIN  
  process( Enable, Read, Addr)  
  begin  
    if Enable = '1' then  
      if( Read = '1' ) then  
        data <= memory(addr);  
      else Data <= "ZZZZZZZZ";  
      end if;  
    else Data <= "ZZZZZZZZ";  
    end if;  
  end process;  
END rom;  
-----
```

پردازنده های خاص

در این بخش تفاوت بین مدل های ماشینهای حالت با مسیر داده توکار و مدل ماشین حالت با مسیر داده مجزا را نشان می دهد. از زاویه طراحی در سطح انتقال ثبات هر طرح دیجیتال شامل یک واحد کنترل (FSM) و یک مسیر داده است.

مسیر داده شامل واحدهای حافظه مانند ثباتها و حافظه و واحدهای ترکیبی مانند: محاسبه و منطق-جمع کننده-ضرب کننده-ثبات انتقالی و مقایسه کننده می باشد.

مسیر داده عملوند را از واحد حافظه بر می دارد و با استفاده از واحدهای ترکیبی عملیات محاسباتی را انجام می دهد و حاصل را به حافظه باز می گرداند. این فرآیند یک یا دو کلاک طول می کشد.

محاسبه کننده ب.م.م ترکیبی

```
-----  
-- Example(5-34):Behvaior Design of GCD calculator  
-- GCD algorithm behavior modeling (combinational)  
-----
```

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
use work.all;
```

```
-----  
entity gcd1 is  
port ( Data_X: in unsigned(3 downto 0);  
       Data_Y: in unsigned(3 downto 0);  
       Data_out: out unsigned(3 downto 0)  
);  
end gcd1;  
-----  
architecture behv of gcd1 is  
begin  
  process(Data_X, Data_Y)  
    variable tmp_X, tmp_Y: unsigned(3 downto 0);  
  begin  
    tmp_X := Data_X;  
    tmp_Y := Data_Y;  
    for i in 0 to 15 loop  
      if (tmp_X/=tmp_Y) then  
        if (tmp_X < tmp_Y) then  
          tmp_Y := tmp_Y - tmp_X;  
        else  
          tmp_X := tmp_X - tmp_Y;  
        end if;  
      else  
        Data_out <= tmp_X;  
      end if;  
    end loop;  
  end process;  
end behv;  
-----
```

طراحی یک ریز پردازنده ساده

Assembly instruct.	First byte	Second byte	Operation
MOV Rn, direct	0000 Rn	direct	$Rn = M(\text{direct})$
MOV direct, Rn	0001 Rn	direct	$M(\text{direct}) = Rn$
MOV @Rn, Rm	0010 Rn	Rm	$M(Rn) = Rm$
MOV Rn, #immed.	0011 Rn	immediate	$Rn = \text{immediate}$
ADD Rn, Rm	0100 Rn	Rm	$Rn = Rn + Rm$
SUB Rn, Rm	0101 Rn	Rm	$Rn = Rn - Rm$
JZ Rn, relative	0110 Rn	relative	$PC = PC + \text{relative}$ (only if Rn is 1)


opcode
operands

$M(Rn) = Rm$


شکل ۵-۶) قالب دستورالعمل های ریز پردازنده

Control Unit

Data Path

 

شکل ۵-۷) بلوک دیاگرام ریزپردازنده

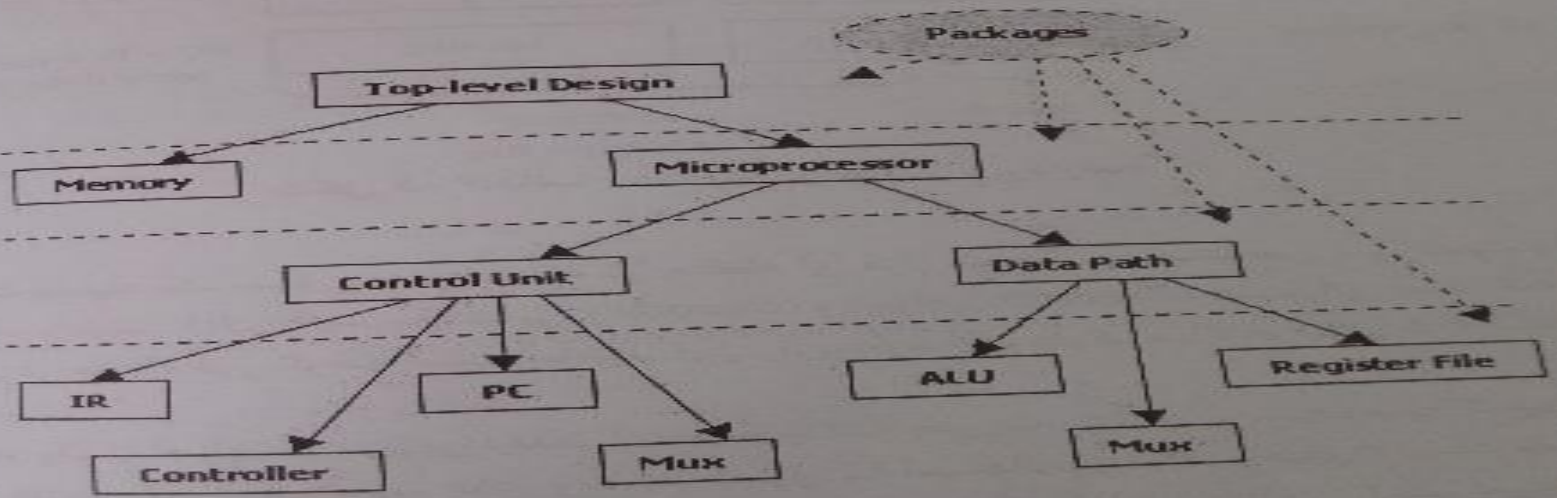

شکل ۵-۸) نمودار سلسله مراتبی ریزپردازنده

انتخاب کننده

```
-----  
-- Simple Microprocessor Design  
-- multiplexor of datapath unit (smallmux.vhd)  
-- three 16 bit inputs and one 16 bit output  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
-----  
entity smallmux is  
port(  
    I0:    in std_logic_vector(15 downto 0);  
    I1:    in std_logic_vector(15 downto 0);  
    I2:    in std_logic_vector(15 downto 0);  
    Sel:   in std_logic_vector(1 downto 0);  
    O:     out std_logic_vector(15 downto 0)  
);  
end smallmux;  
-----  
architecture behv of smallmux is  
begin  
    process(I0, I1, I2, Sel)  
    begin  
        case Sel is  
            when "00" =>          O <= I0;  
            when "01" =>          O <= I1;  
            when "10" =>          O <= I2;  
            when others =>  
                end case;  
        end process;  
    end behv;  
-----
```

بافر خروجی

```
-----  
-- Simple Microprocessor Design  
-- Output buffer of Data Path (obuf.vhd)  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
use work.constant_lib.all;  
-----  
entity obuf is  
port( O_en:          in std_logic;  
      obuf_in:       in std_logic_vector(15 downto 0);  
      obuf_out:      out std_logic_vector(15 downto 0)  
    );  
end obuf;  
-----  
architecture behv of obuf is  
begin  
  process (O_en, obuf_in)  
  begin  
    if O_en = '1' then  
      obuf_out <= obuf_in;  
    else  
      obuf_out <= HIRES;  
    end if;  
  end process;  
end behv;  
-----
```

ثبات دستور العمل

```
-----  
-- Simple Microprocessor Design  
-- Instruction Register (IR.vhd)  
-----  
library      ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
use ieee.std_logic_unsigned.all;  
-----  
entity IR is  
port( IRin:      in std_logic_vector(15 downto 0);  
      IRld:      in std_logic;  
      dir_addr:  out std_logic_vector(15 downto 0);  
      IRout:     out std_logic_vector(15 downto 0)  
      );  
end IR;  
-----  
architecture behv of IR is  
begin  
  process(IRld, IRin)  
  begin  
    if IRld = '1' then  
      IRout <= IRin;  
      dir_addr <= "00000000" & IRin(7 downto 0);  
    end if;  
  end process;  
end behv;  
-----
```

موفق و پیروز باشید

ز کوشش به هر چیز خواهی رسید
به هر چیز خواهی کماهی رسید
برو کارگر باش و امیدوار
که از یاس جز مرگ ناید به بار
گرت پایدار است در کارها
شود سهل پیش تو دشوارها

پایان